

Beispiel A1:

$U_1 = -9 \text{ V}$	$U_4 = 6 \text{ V}$
$U_2 = 0 \text{ V}$	$U_5 = 9,99 \text{ V}$
$U_3 = 10,8 \text{ V}$	$U_6 = 6 \text{ V}$

Beispiel B1:

$U_1 = 18 \text{ V}$	$U_4 = 0 \text{ V}$
$U_2 = 21,6 \text{ V}$	$U_5 = 12 \text{ V}$
$U_3 = 19,98 \text{ V}$	$U_6 = 12 \text{ V}$